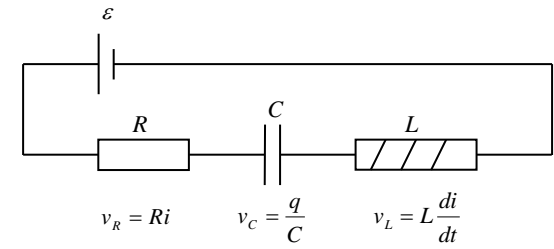


Kap 30 Induktans

Potensialf all over ulike komponente r

$$v_R = Ri \quad v_C = \frac{q}{C} \quad v_L = L \frac{di}{dt} \quad i = \frac{dq}{dt}$$



$$\varepsilon - Ri - \frac{q}{C} - L \frac{di}{dt} = 0$$

RC - krets Tidskonstant: $\tau = RC$

Lading : $\varepsilon - Ri - \frac{q}{C} = 0 \quad q = C\varepsilon(1 - e^{-t/RC}) \quad i = \frac{\varepsilon}{R} e^{-t/RC}$

Utlading : $-Ri - \frac{q}{C} = 0 \quad q = Q_0 e^{-t/RC} \quad i = -\frac{Q_0}{RC} e^{-t/RC} = -\frac{V_C}{R} e^{-t/RC} = I_0 e^{-t/RC}$

RL - krets Tidskonstant: $\tau = \frac{L}{R}$

$$\varepsilon - Ri - L \frac{di}{dt} = 0 \quad i = \frac{\varepsilon}{R} (1 - e^{-\frac{R}{L}t})$$

$$-Ri - L \frac{di}{dt} = 0 \quad i = I_0 e^{-\frac{R}{L}t}$$

LC - krets

$$-L \frac{di}{dt} - \frac{q}{C} = 0 \quad q = Q_0 \cos(\omega t + \varphi) \quad i = -\omega Q_0 \sin(\omega t + \varphi)$$

$$\omega = \sqrt{\frac{1}{LC}} \quad f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} \quad T = \frac{2\pi}{\omega} = 2\pi \sqrt{LC}$$

LRC - krets

$$-Ri - L \frac{di}{dt} - \frac{q}{C} = 0 \quad q = Q_0 e^{-\frac{R}{2L}t} \cos(\omega t + \varphi)$$

$$\omega = \sqrt{\omega_0^2 - \frac{R^2}{4L^2}} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \quad T = \frac{2\pi}{\omega} = 2\pi \frac{1}{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}$$

R : [Ω]


C : [F]

L : [H]

Kap 30 Induktans (forts.)

Potensialfall over ulike komponenter
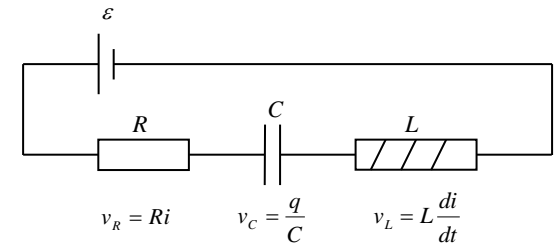
$$v_R = Ri \quad v_C = \frac{q}{C} \quad v_L = L \frac{di}{dt} \quad i = \frac{dq}{dt}$$



$$\varepsilon - Ri - \frac{q}{C} - L \frac{di}{dt} = 0$$





RC - krets Tidskonstant: $\tau = RC$

Lading:

$$\varepsilon - Ri - \frac{q}{C} = 0$$

$$q = C\varepsilon(1 - e^{-t/RC})$$

$$i = \frac{\varepsilon}{R} e^{-t/RC}$$


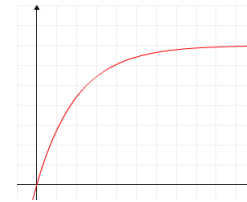
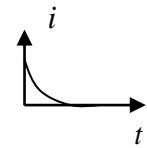
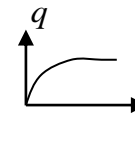
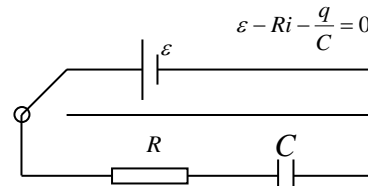


Utlading:

$$-Ri - \frac{q}{C} = 0$$

$$q = Q_0 e^{-t/RC}$$

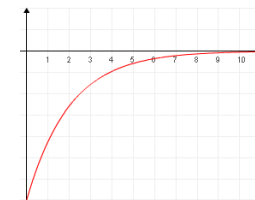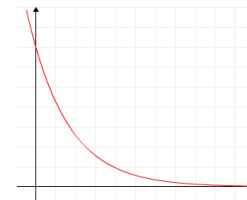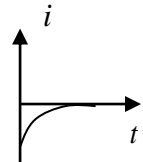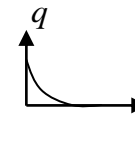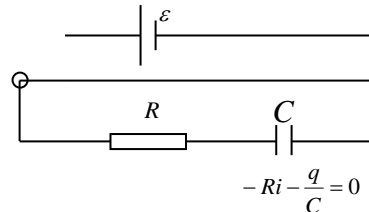
$$i = -\frac{Q_0}{RC} e^{-t/RC} = -\frac{V_C}{R} e^{-t/RC} = I_0 e^{-t/RC}$$



Kap 30 Induktans (forts.)

Potensialf all over ulike komponente r


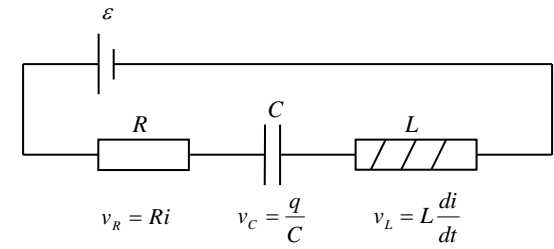
$$v_R = Ri \quad v_C = \frac{q}{C} \quad v_L = L \frac{di}{dt} \quad i = \frac{dq}{dt}$$




$$\varepsilon - Ri - \frac{q}{C} - L \frac{di}{dt} = 0$$

RL - krets Tidskonstant: $\tau = \frac{L}{R}$

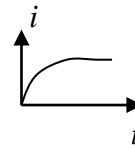
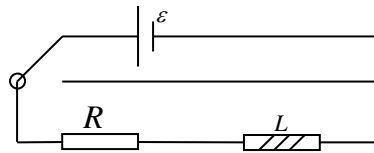
$$\varepsilon - Ri - L \frac{di}{dt} = 0 \quad i = \frac{\varepsilon}{R} (1 - e^{-\frac{R}{L}t})$$



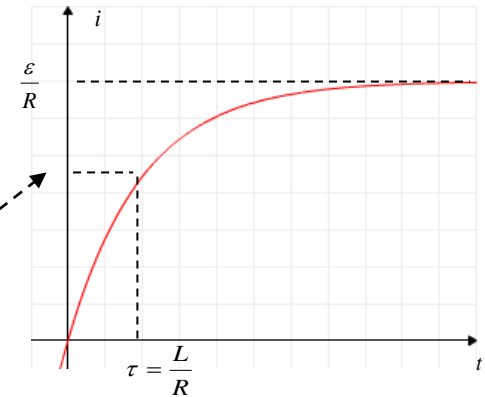
$$i = \frac{\varepsilon}{R} (1 - e^{-\frac{R}{L}t}) = \frac{\varepsilon}{R} (1 - e^{-\frac{RL}{LR}}) = \frac{\varepsilon}{R} (1 - e^{-1}) = \frac{\varepsilon}{R} (1 - \frac{1}{e})$$


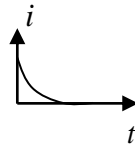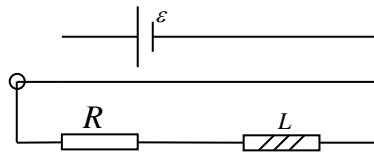
$$-Ri - L \frac{di}{dt} = 0 \quad i = I_0 e^{-\frac{R}{L}t}$$


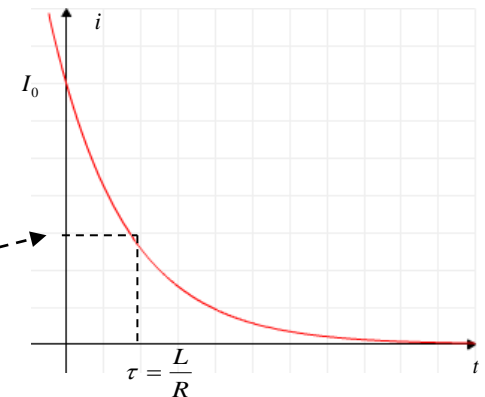
$$i = I_0 e^{-\frac{R}{L}t} = I_0 e^{-\frac{RL}{LR}} = I_0 e^{-1} = \frac{1}{e} I_0$$




Stabil strøm (med batteri påkoblet) vil si strøm ved $t = \infty$, dvs $i = \frac{\varepsilon}{R}$

Kap 30 Induktans (forts.)

Potensialf all over ulike komponente r
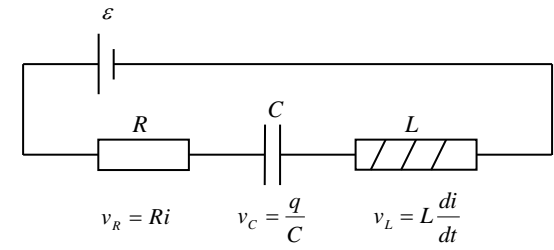
$$v_R = Ri \quad v_C = \frac{q}{C} \quad v_L = L \frac{di}{dt} \quad i = \frac{dq}{dt}$$






$$\varepsilon - Ri - \frac{q}{C} - L \frac{di}{dt} = 0$$

LC - krets

$$-L \frac{di}{dt} - \frac{q}{C} = 0 \quad q = Q_0 \cos(\omega t + \varphi) \quad i = -\omega Q_0 \sin(\omega t + \varphi)$$

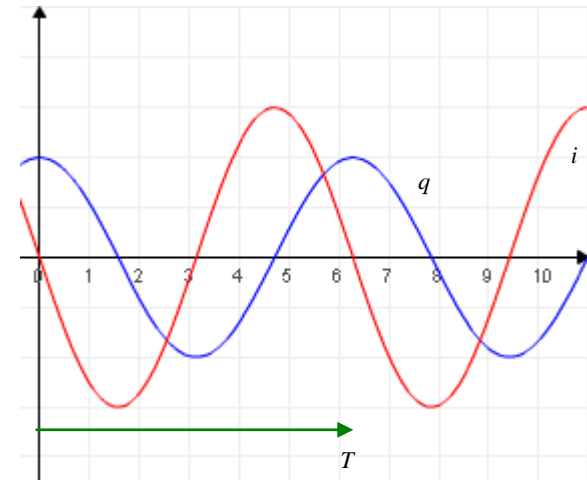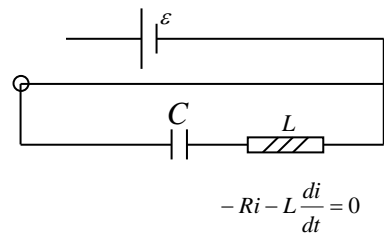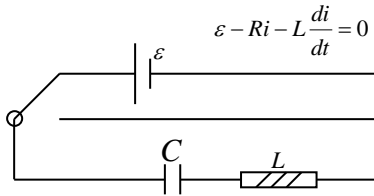
$$\omega = \sqrt{\frac{1}{LC}} \quad f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} \quad T = \frac{2\pi}{\omega} = 2\pi \sqrt{LC}$$



Kap 30 Induktans (forts.)

Potensialfall over ulike komponenter
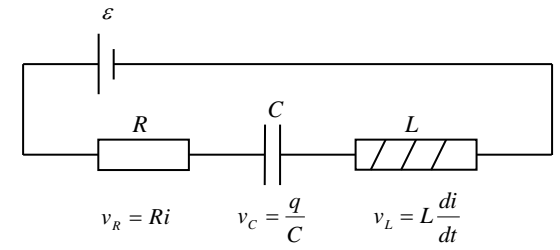
$$v_R = Ri \quad v_C = \frac{q}{C} \quad v_L = L \frac{di}{dt} \quad i = \frac{dq}{dt}$$







$$\varepsilon - Ri - \frac{q}{C} - L \frac{di}{dt} = 0$$

LRC - krets


$$-Ri - L \frac{di}{dt} - \frac{q}{C} = 0 \quad q = Q_0 e^{\frac{R}{2L}t} \cos(\omega t + \varphi)$$

$$\omega = \sqrt{\omega_0^2 - \frac{R}{4L^2}} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

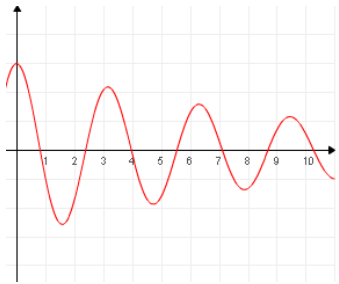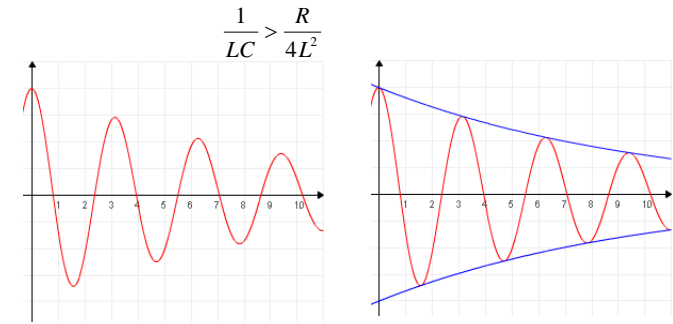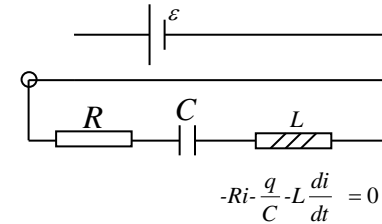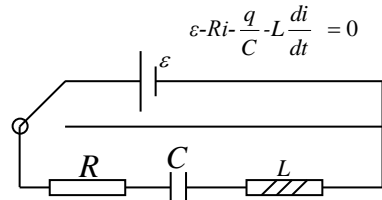
$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R}{4L^2}} \quad T = \frac{2\pi}{\omega} = 2\pi \frac{1}{\sqrt{\frac{1}{LC} - \frac{R}{4L^2}}}$$



$$\frac{1}{LC} > \frac{R}{4L^2}$$

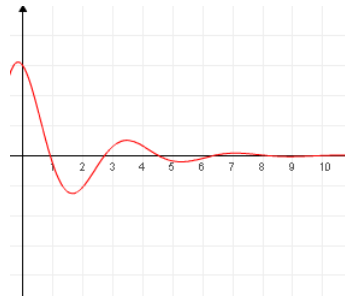

$$\frac{1}{LC} > \frac{R}{4L^2}$$

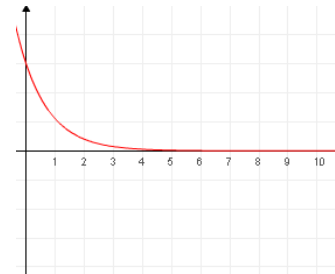

$$\frac{1}{LC} = \frac{R}{4L^2}$$



$$\frac{1}{LC} < \frac{R}{4L^2}$$

Kap 30 Induktans (forts.)

Gjensidig induktans

$$\varepsilon_2 = -M \frac{di_1}{dt} \quad \varepsilon_1 = -M \frac{di_2}{dt}$$

$$M = \frac{N_2 \Phi_{B2}}{i_1} = \frac{N_1 \Phi_{B1}}{i_2}$$

